

CogniChip Hackathon Tutorial



1. Log in Cognichip Platform (<https://members.cognichip.ai/>)

The screenshot displays the Cognichip Member Portal interface. On the left, a sidebar contains a 'Profile' button and a 'Manage Retention Policy' link. The main content area features a user profile for 'Weihua Xiao' with the email 'weihua.xiao@nyu.edu'. Below the profile, there are three sections: 'Personal Information', 'Security Settings', and 'Account Information'. The 'Personal Information' section includes fields for First Name (Weihua), Last Name (Xiao), Email Address (weihua.xiao@nyu.edu), Company (Cognichip), Country (Select Country), and Time Zone (Select Time Zone), with a 'Save Changes' button. The 'Security Settings' section has a 'Change Password' button and a 'Download the Beta app' section with a checkbox for agreeing to the Cognichip 'Cloud Services Agreement' and buttons for 'Mac Download' and 'Windows Download'. The 'Account Information' section shows the Username (weihua.xiao), Member Since (November 2025), Account Type (Designer 0.1), and Last Login (0 seconds ago).

2. Download CogniChip

This screenshot is a closer view of the Cognichip Member Portal, focusing on the 'Download the Beta app' section. The user profile 'Weihua Xiao' is visible at the top. The 'Personal Information' section is partially visible on the left. The 'Security Settings' section is on the right, featuring a 'Change Password' button. The 'Download the Beta app' section is highlighted with a white border and contains a checkbox for agreeing to the Cognichip 'Cloud Services Agreement' for this extension, along with 'Mac Download' and 'Windows Download' buttons. Below this, a link says 'For the full list of downloadable artifacts, please Click here'. The 'Account Information' section is at the bottom, showing the Username (weihua.xiao), Member Since (November 2025), Account Type (Designer 0.1), and Last Login (0 seconds ago).

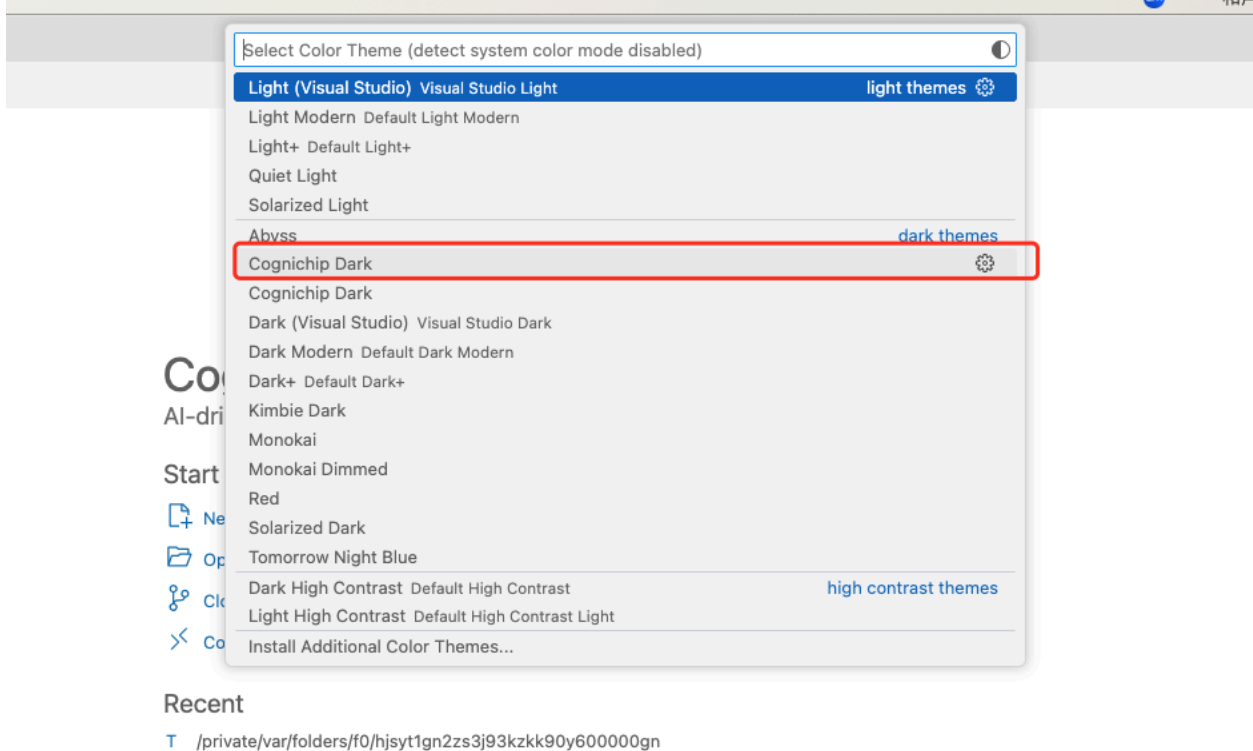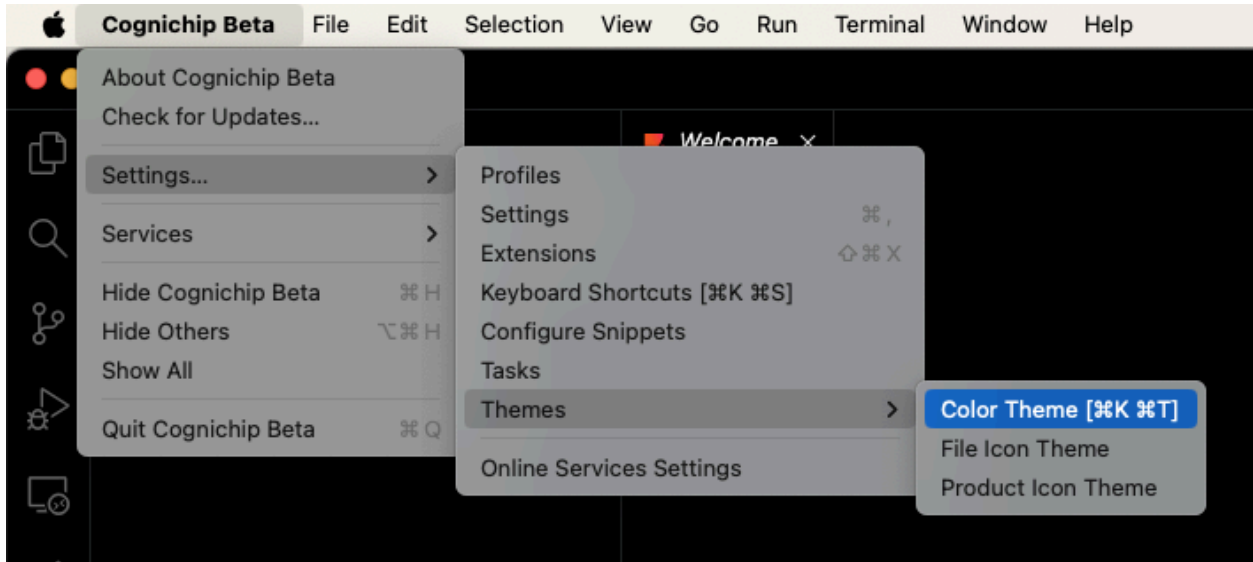3. Use CogniChip:
 - a. Create project folder
 - b. Open CogniChip & Set color theme



- c. Open project folder

Cognichip Beta

AI-driven semiconductor design

Start

New File...

Open...

Clone Git Repository...

Connect to...

d. Start chat for hardware design

- Generate the verilog code

CHAT

Can you generate the verilog code for a 8-bit Kogge-Stone adder?

Completed thinking 4s

I'll create an 8-bit Kogge-Stone adder for you. Let me explain the design strategy first:

Design Approach:
The Kogge-Stone adder is a parallel prefix adder that achieves fast addition through:

- **Stage 0:** Computing initial generate (G) and propagate (P) signals for each bit
- **Stages 1-3:** Using $\log_2(8) = 3$ stages of prefix computation to propagate carries in parallel
- **Final Stage:** Computing the sum bits using the propagated carry signals

The key advantage is $O(\log n)$ depth with maximum parallelism, making it one of the fastest adder architectures.

Let me write the RTL code:

Created kogge_stone_adder_8bit.v

Completed thinking 1s

Now let me run the linter to check the code:

Listed files

Completed thinking 1s

Excellent! I've successfully created the 8-bit Kogge-Stone adder with clean syntax.

What was implemented:

- 3-stage parallel prefix network for 8-bit operands ($\log_2(8) = 3$ stages)
- Stage 0: Computes initial generate (G) and propagate (P) signals
- Stages 1-3: Progressive prefix computation with spans of 1, 2, and 4 bits
- Carry-in support with proper propagation through all stages
- Carry-out generation from the final stage signals
- Optimized for speed with maximum parallelism in carry computation

The design is fully combinational and provides fast addition with minimal critical path delay. The linter confirmed no syntax or style issues.

What would you like to work on next? Would you like me to:

- Create a testbench for this adder?
- Generate a DEPS.yml file for simulation setup?
- Explain any part of the implementation in more detail?
- Create a parameterized version for different bit widths?

Welcomekogge_stone_adder_8bit.v X

F kogge_stone_adder_8bit.v

```
1 // 8-bit Kogge-Stone Adder
2 // Fast parallel prefix adder with O(log n) depth
3 // Author: Cognichip Co-Designer
4 // Description: Implements Kogge-Stone algorithm for 8-bit addition
5
6 module kogge_stone_adder_8bit (
7     input logic [7:0] a, // First 8-bit operand
8     input logic [7:0] b, // Second 8-bit operand
9     input logic cin, // Carry input
10    output logic [7:0] sum, // 8-bit sum output
11    output logic cout, // Carry output
12);
13
14 // Generate and Propagate signals for each stage
15 logic [7:0] g0, p0; // Stage 0: Initial G and P
16 logic [7:0] g1, p1; // Stage 1: After first prefix level
17 logic [7:0] g2, p2; // Stage 2: After second prefix level
18 logic [7:0] g3, p3; // Stage 3: After third prefix level (final)
19
20 // Carry signals
21 logic [7:0] c; // Carry into each bit position
22
23 // =====
24 // Stage 0: Initial Generate and Propagate
25 // =====
26 // Generate: G[i] = a[i] & b[i]
27 // Propagate: P[i] = a[i] ^ b[i]
28 always_comb begin
29     for (int i = 0; i < 8; i++) begin
30         g0[i] = a[i] & b[i];
31         p0[i] = a[i] ^ b[i];
32     end
33 end
34
35 // =====
36 // Stage 1: First prefix level (span = 1)
37 // =====
38 // Combines adjacent pairs
39 always_comb begin
40     // Bit 0 stays the same
41     g1[0] = g0[0];
42     p1[0] = p0[0];
43
44     // Bits 1-7: combine with previous bit
45     for (int i = 1; i < 8; i++) begin
46         g1[i] = g0[i] | (p0[i] & g0[i-1]);
47         p1[i] = p0[i] & p0[i-1];
48     end
49 end
50
51 // =====
52 // Stage 2: Second prefix level (span = 2)
53 // =====
54 // Combines pairs with span of 2
55 always_comb begin
56     // Bits 0-1 stay the same
```

PROBLEMS OUTPUT TERMINAL PORTS

- Generate the testbench code

can you next generate the testbench code for this adder?

Completed thinking 6s

Perfect! Let me create a comprehensive testbench for the 8-bit Kogge-Stone adder.

Verification Strategy:

I'll implement a thorough testbench that covers:

1. Edge Cases: All zeros, all ones, boundary values

2. Carry Propagation: Test cases that stress the parallel prefix network

3. Carry-In Variations: Test with cin = 0 and cin = 1

4. Random Tests: Multiple random inputs to explore the state space

5. Corner Cases: Maximum values, overflow scenarios

6. Golden Reference: Compare against SystemVerilog's native addition for verification

Let me write the testbench:

Created tb_kogge_stone_adder_8bit.sv

Completed thinking 1s

Now let me lint the testbench:

Linted files

Completed thinking 2s

Let me fix those lint warnings by adding the proper arguments to \$finish and \$fatal:

Edited tb_kogge_stone_adder_8bit.sv

Completed thinking 1s

Let me re-run the linter to confirm the warnings are resolved:

Linted files

Completed thinking 3s

Excellent! The testbench is ready and lints cleanly with no issues.

What I've created:

A comprehensive testbench with 10 test categories covering:

1. Edge Cases: All zeros with/without carry-in

2. Single Bit Additions: Basic 1+1 scenarios

3. Maximum Values: 0xFF additions, overflow testing

4. Carry Propagation: Long carry chains, alternating bit patterns

5. Power-of-2 Values: 1, 2, 4, 8, 16, 32, 64, 128 combinations

6. Mid-Range Values: Various hexadecimal patterns (0x55, 0xAA, etc.)

7. Sequential Increments: Systematic testing of 0-15 increments

8. Random Tests: 50 randomized test cases

9. Boundary Transitions: Testing around 0x7F/0x80 boundary

10. Carry-In Combinations: Testing both cin=0 and cin=1 variants

Test Features:

1. Edge Cases: All zeros with/without carry-in

2. Single Bit Additions: Basic 1+1 scenarios

3. Maximum Values: 0xFF additions, overflow testing

4. Carry Propagation: Long carry chains, alternating bit patterns

5. Power-of-2 Values: 1, 2, 4, 8, 16, 32, 64, 128 combinations

6. Mid-Range Values: Various hexadecimal patterns (0x55, 0xAA, etc.)

7. Sequential Increments: Systematic testing of 0-15 increments

8. Random Tests: 50 randomized test cases

9. Boundary Transitions: Testing around 0x7F/0x80 boundary

10. Carry-In Combinations: Testing both cin=0 and cin=1 variants

E: tb_kogge_stone_adder_8bit.sv

1 // Testbench for 8-bit Kogge-Stone Adder

2 // Author: Copchip Co-Designer

3 // Description: Comprehensive verification of Kogge-Stone adder functionality

4

5 module tb_kogge_stone_adder_8bit;

6

7 // Testbench signals

8 logic [7:0] a;

9 logic [7:0] b;

10 logic cin;

11 logic [7:0] sum;

12 logic cout;

13

14 // Golden reference signals

15 logic [8:0] expected_result;

16 logic [7:0] expected_sum;

17 logic expected_cout;

18

19 // Test statistics

20 int test_count;

21 int pass_count;

22 int fail_count;

23

24 // =====

25 // OUT Instantiation

26 // =====

27 kogge_stone_adder_8bit dut (

28 .a(a),

29 .b(b),

30 .cin(cin),

31 .sum(sum),

32 .cout(cout)

33);

34

35 // =====

36 // Golden Reference Model

37 // =====

38 always_comb begin

39 expected_result = (1'b0, a) + (1'b0, b) + (0'b0, cin);

40 expected_sum = expected_result[7:0];

41 expected_cout = expected_result[8];

42 end

43

44 // =====

45 // Test Task: Check Result

46 // =====

47 task automatic check_result(string test_name);

48 test_count++;

49

50 // Wait for combinational logic to settle

51 #1;

52

53 if (sum == expected_sum && cout == expected_cout) begin

54 pass_count++;

55 \$display("LOG: %01 : INFO : %0k_kogge_stone_adder_8bit : dut.sum : expected_value: 8'h%h actual_value: 8'h%h",

● Generate .yaml for simulation

A comprehensive testbench with 10 test categories covering:

1. Edge Cases: All zeros with/without carry-in

2. Single Bit Additions: Basic 1+1 scenarios

3. Maximum Values: 0xFF additions, overflow testing

4. Carry Propagation: Long carry chains, alternating bit patterns

5. Power-of-2 Values: 1, 2, 4, 8, 16, 32, 64, 128 combinations

6. Mid-Range Values: Various hexadecimal patterns (0x55, 0xAA, etc.)

7. Sequential Increments: Systematic testing of 0-15 increments

8. Random Tests: 50 randomized test cases

9. Boundary Transitions: Testing around 0x7F/0x80 boundary

10. Carry-In Combinations: Testing both cin=0 and cin=1 variants

Test Features:

• Golden reference model using native SystemVerilog addition

• Automatic result checking with detailed error reporting

• Proper logging format as specified

• Test statistics summary (pass/fail counts)

• Timeout watchdog protection

• FST waveform dumping for VaporView analysis

• Clear TEST PASSED/TEST FAILED reporting

The testbench will run approximately 100+ test vectors to thoroughly validate the Kogge-Stone adder's parallel prefix computation.

Ready for simulation! Would you like me to run the simulation now?

please create the corresponding .yaml file for later simulation.

Completed thinking 3s

Perfect! Let me create the DEPS.yaml file for simulating the Kogge-Stone adder testbench.

Created DEPS.yaml

Completed thinking 1s

Excellent! I've created the DEPS.yaml file for your Kogge-Stone adder project.

DEPS Configuration Details:

• Target name: kogge_stone_adder_sim

• Dependencies:

◦ kogge_stone_adder_8bit.sv (design module - loaded first)

◦ tb_kogge_stone_adder_8bit.sv (testbench - loaded second)

• Top module: tb_kogge_stone_adder_8bit (the testbench)

The configuration follows proper dependency order with the DUT loaded before the testbench, ensuring clean compilation.

Your project is now complete and ready for simulation!

You have:

✔ Design: kogge_stone_adder_8bit.sv (8-bit Kogge-Stone parallel prefix adder)

✔ Testbench: tb_kogge_stone_adder_8bit.sv (comprehensive verification with 100+ test vectors)

✔ DEPS: DEPS.yaml (simulation configuration)

Would you like me to run the simulation now to verify the adder functionality?

3 // Description: Simulation dependencies for Kogge-Stone adder testbench

4

5 // Testbench simulation target

6 kogge_stone_adder_sim:

7 deps:

8 - kogge_stone_adder_8bit.sv

9 - tb_kogge_stone_adder_8bit.sv

10 top: tb_kogge_stone_adder_8bit

11

PROBLEMS

OUTPUT

TERMINAL

PORTS

eval export HOMEBREW_PREFIX="/opt/homebrew";

export HOMEBREW_CELLAR="/opt/homebrew/Cellar";

- Do simulation: set the target name & add files (verilog files, testbench files, .yaml)

Simulate Re-run ▶

Test your chip design in a virtual environment, validating behavior, performance, and logic before physical implementation.

Run targeted scenarios, catch design flaws early, and gain confidence in how your system will perform under real-world conditions.

Job Name **70AF3335**

Target **kogge_stone_adder_sim** + New Deps

Use OpenCos command ☐

Total files: 3

Total size: 13267 bytes

Files + Add files

- DEPS.yml
- kogge_stone_adder_8bit.sv
- tb_kogge_stone_adder_8bit.sv

✓ **Completed** E2156EE2


Save waveform

History ▾


Stdout ▾

Stderr ▾

- Save .fst waveform file & visualize

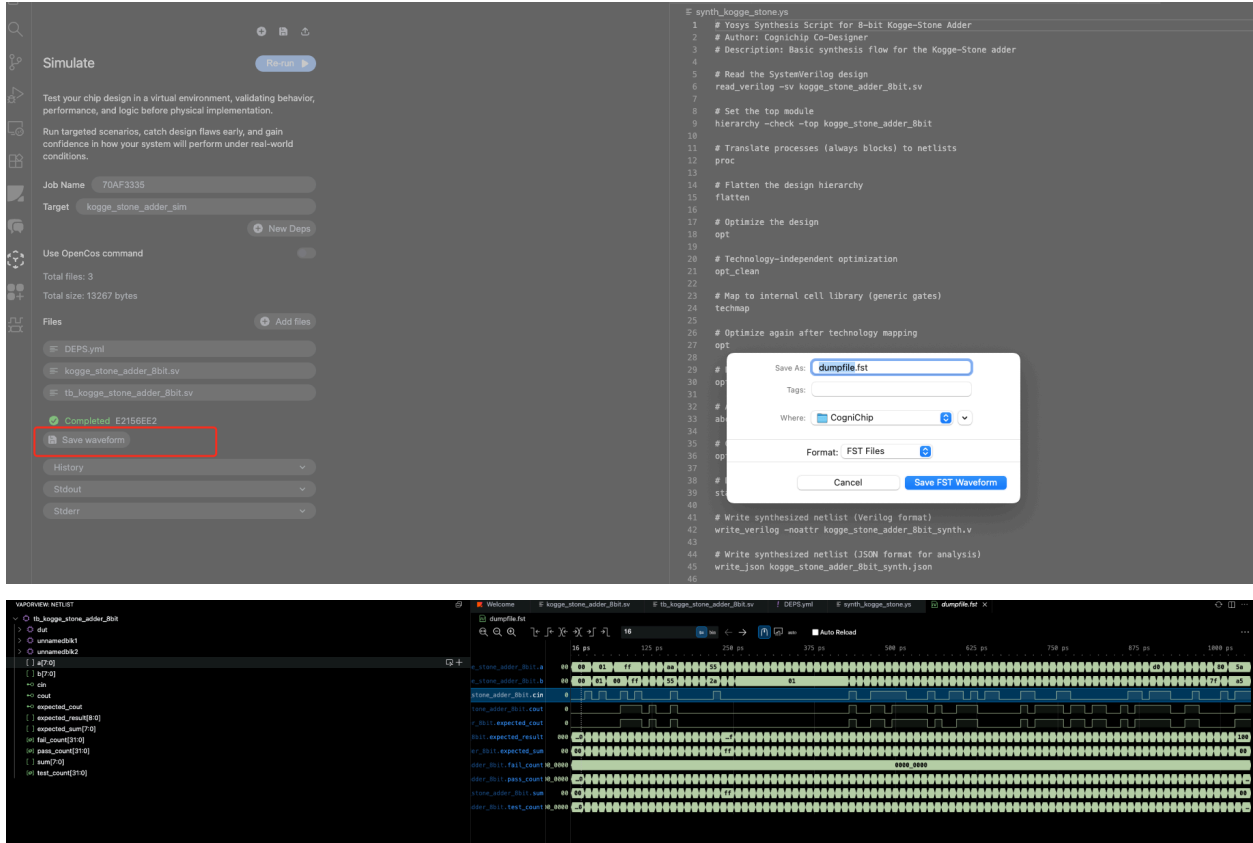

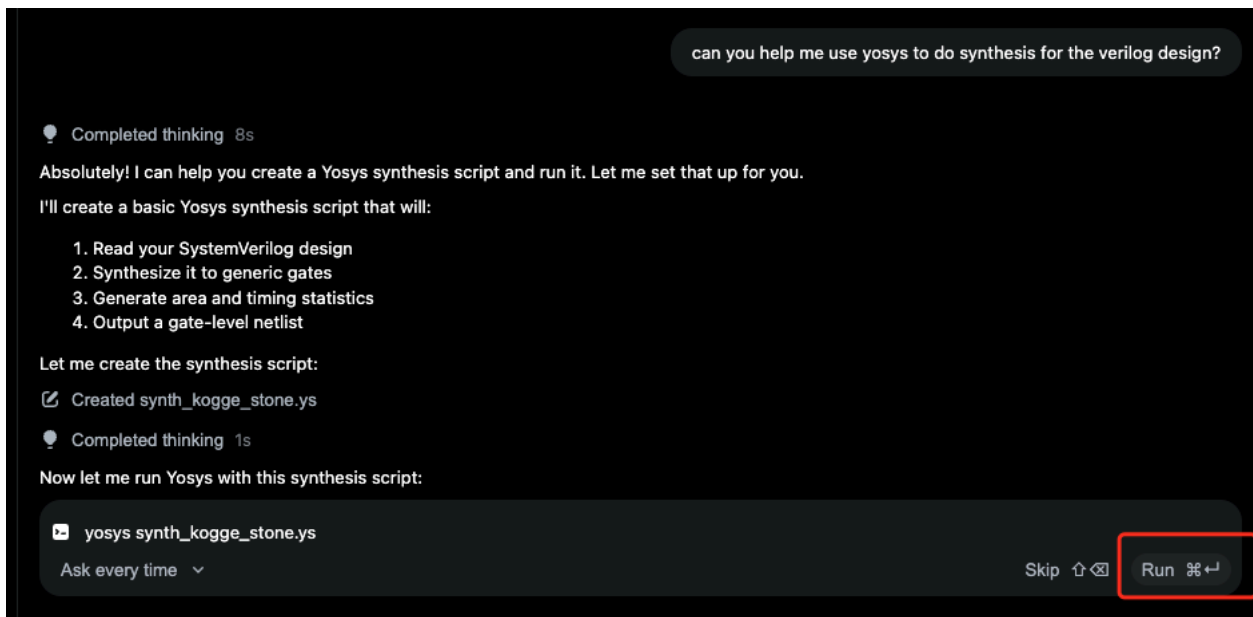- Download yosys (mac: brew install yosys; linux: sudo apt-get install yosys)
- Use yosys to do synthesis for the verilog design



Welcome kogge_stone_adder_8bit.sv tb_kogge_stone_adder_8bit.sv ! DEPS.yml synth_kogge_stone.ys × dumpfile.fst

synth_kogge_stone.ys

```
1  # Yosys Synthesis Script for 8-bit Kogge-Stone Adder
2  # Author: Cognichip Co-Designer
3  # Description: Basic synthesis flow for the Kogge-Stone adder
4
5  # Read the SystemVerilog design
6  read_verilog -sv kogge_stone_adder_8bit.sv
7
8  # Set the top module
9  hierarchy -check -top kogge_stone_adder_8bit
10
11 # Translate processes (always blocks) to netlists
12 proc
13
14 # Flatten the design hierarchy
15 flatten
16
17 # Optimize the design
18 opt
19
20 # Technology-independent optimization
21 opt_clean
22
23 # Map to internal cell library (generic gates)
24 techmap
25
26 # Optimize again after technology mapping
27 opt
28
29 # Perform area optimization
30 opt_clean
31
32 # ABC optimization for logic synthesis
33 abc -g AND,OR,XOR,NAND,NOR
34
35 # Clean up after ABC
36 opt_clean
37
38 # Display statistics
39 stat
40
41 # Write synthesized netlist (Verilog format)
42 write_verilog -noattr kogge_stone_adder_8bit_synth.v
43
44 # Write synthesized netlist (JSON format for analysis)
45 write_json kogge_stone_adder_8bit_synth.json
46
47 # Optional: Write graphical representation
48 # show -format dot -prefix kogge_stone_adder_graph
49
```

Now let me run Yosys with this synthesis script:

```
Ran: yosys synth_kogge_stone.js
13.1. Executing BRUAMAP pass.

13.2. Executing DEMUXMAP pass.
Dumping module `kogge_stone_adder_8bit'.

14. Executing JSON backend.

End of script. Logfile hash: 52df5541ce, CPU: user 0.05s system 0.01s, MEM: 13.09 MB peak
Yosys 0.47 (git sha1 647d61dd9, clang++ 16.0.0 -fPIC -O3)
Time spent: 56% 1x abc (0 sec), 16% 3x read_verilog (0 sec), ...
```

Completed thinking 1s

Perfect! The synthesis completed successfully! Let me show you what was generated:

Checked files

Completed thinking 1s

Excellent! **Synthesis completed successfully!** Here's what we accomplished:

Synthesis Results Summary:

Gate Count:

- **Total cells: 47 gates**
 - AND gates: 7
 - NAND gates: 24
 - OR gates: 7
 - XOR gates: 9

Connectivity:

- **Wires: 44** (72 bits total)
- **Inputs: 17 signals** (a[7:0], b[7:0], cin)
- **Outputs: 9 signals** (sum[7:0], cout)

Generated Files:

- ✓ `kogge_stone_adder_8bit_synth.v` - Synthesized gate-level netlist (Verilog)
- ✓ `kogge_stone_adder_8bit_synth.json` - Synthesis results in JSON format
- ✓ `synth_kogge_stone.js` - Yosys synthesis script

Key Observations:

The Kogge-Stone adder synthesized into a compact **47-gate design** which is quite efficient! The parallel prefix structure is evident in the gate distribution:

- **XOR gates (9):** Used for final sum computation and propagate generation
- **NAND gates (24):** Primary logic for the prefix computation stages
- **AND/OR gates (14):** Generate and combine signals in the prefix tree

Would you like me to: